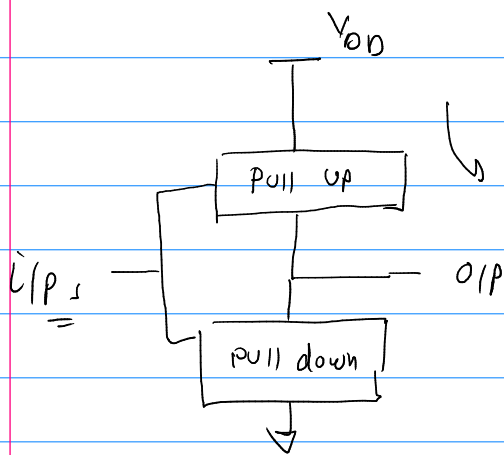


## Lecture # 16

## # Switch. level logic Design.

Pmos  $\rightarrow$  Good conductor for passing logic '1' or  $V_{DD}$

Nmos  $\rightarrow$  Good conductor for passing logic '0' or ground




When pull-up is "ON"  $\Rightarrow$  o/p = '1'

When pull-down is ON  $\Rightarrow$  o/p = '0'

at a time Either pull-up is "ON" or pull-down is ON

PMOS  $\rightarrow$  ON when i/p = '0'

NMOS  $\rightarrow$  ON when i/p = '1'

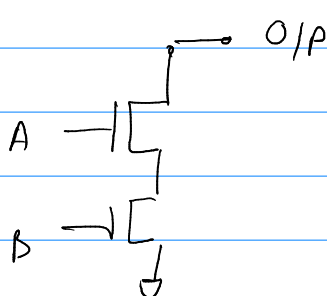


When NMOS transistors (Switches) are in series  $\rightarrow$

$\Rightarrow$  O/p is going to connect with ground terminal only & only when both


$\Rightarrow$  ! (AND)

$\Rightarrow$   $A = B = '1'$

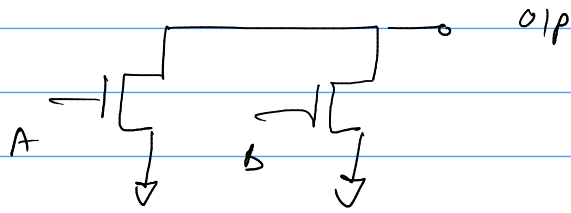


Either 'A' or  
'B' is '1'  
then  $\text{o/p} = \underline{\underline{'0'}}$

$\Rightarrow \neg(A \vee B)$

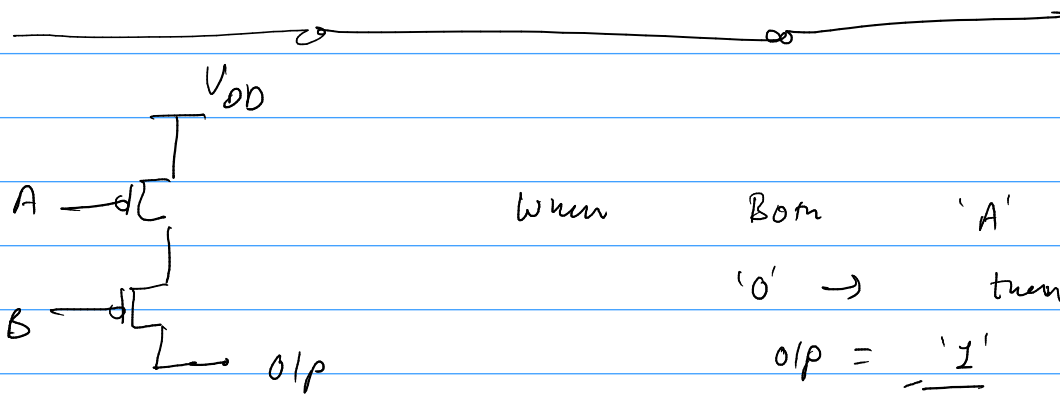


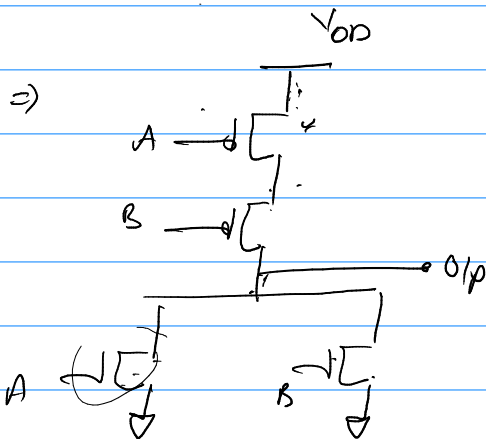When Both 'A' & 'B' are  
'0'  $\rightarrow$  then only  
 $\text{o/p} = \underline{\underline{'1'}}$




NOR GATE

	A	B		o/p
✓	0	0	$\rightarrow$	1
-	0	1	$\rightarrow$	0
-	1	0	$\rightarrow$	0
-	1	1	$\rightarrow$	0

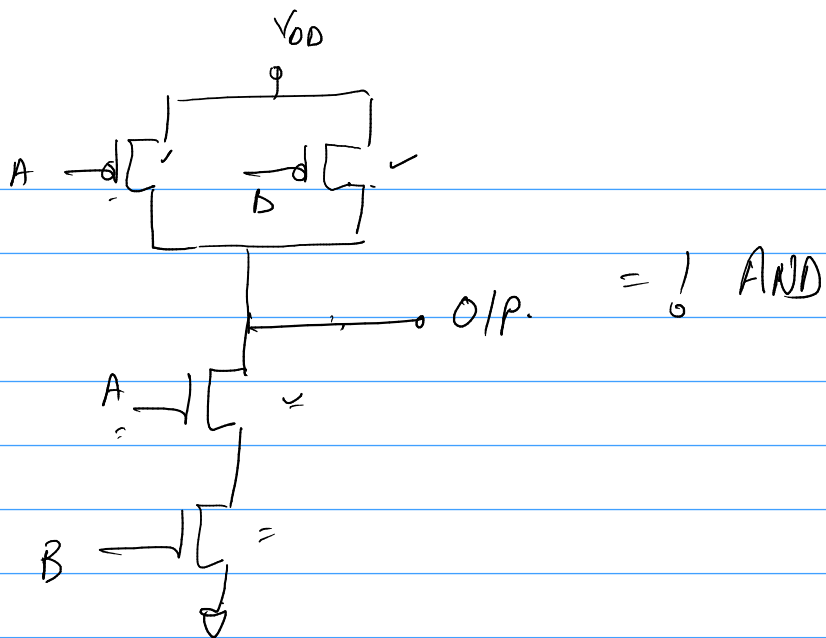

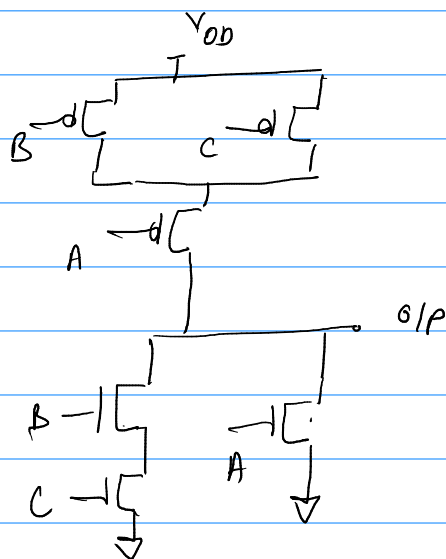
#  $Y = (A + B \cdot C)'$

for  $O/P = 0$   
 ①  $\Rightarrow$  When Both B & C are '1'.  
 or ②  $\Rightarrow A = 1$


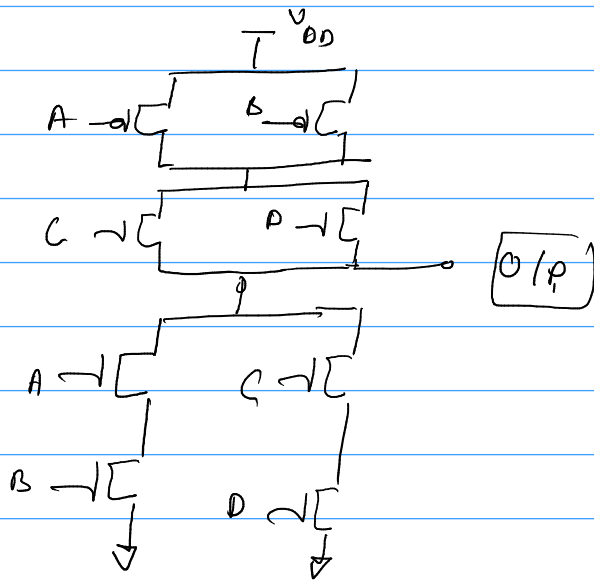
$$Y = \left[ \underbrace{AB} + \underbrace{CD} \right]'$$





$$Y = A + B'C'$$

$$Y' = [A + B'C']' = A' \cdot (B + C)$$

$$Y = \left[ \underbrace{A'} \cdot (B + C) \right]'$$

$$Y = \left[ \begin{array}{l} X \cdot (B + C) \\ X \cdot Y \end{array} \right]'$$

$$A' = X$$

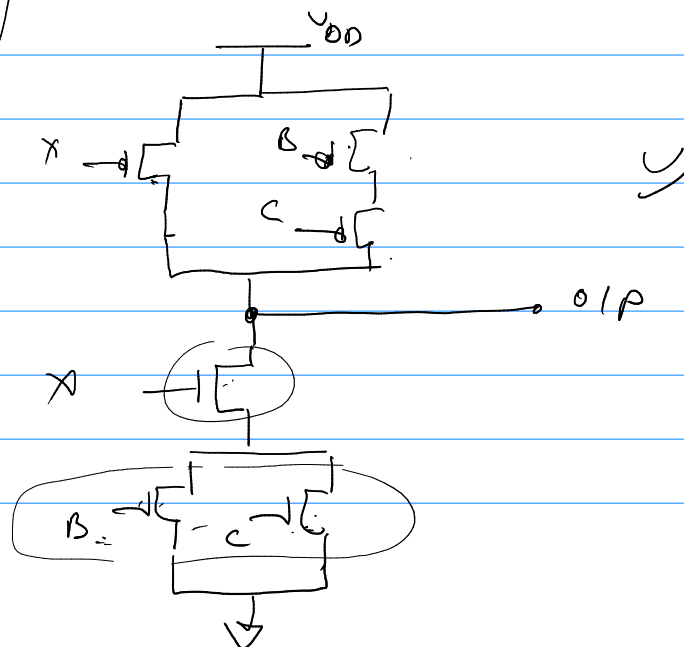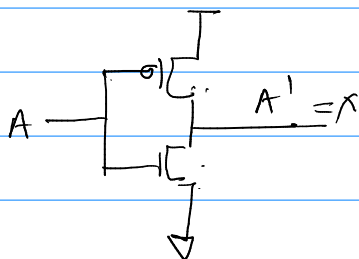


$$Y = \underline{A + B' C'}$$

$$Y' = [A + B' C']'$$




$$B' = \alpha$$

$$C' = \beta$$

$$Y' = [A + \alpha \beta]'$$

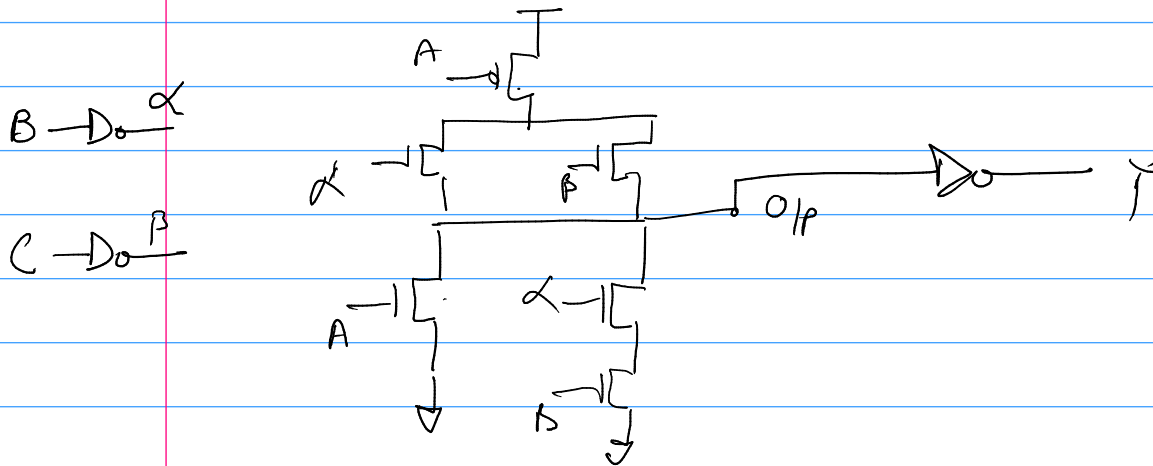

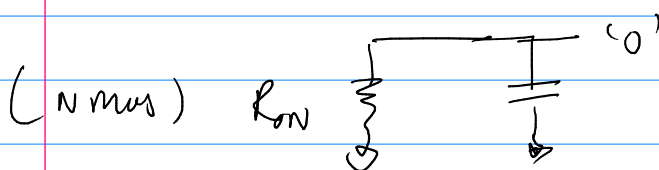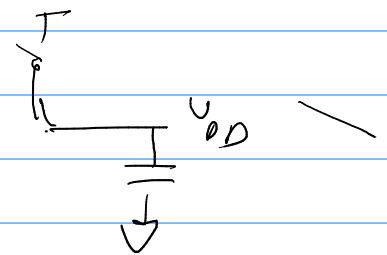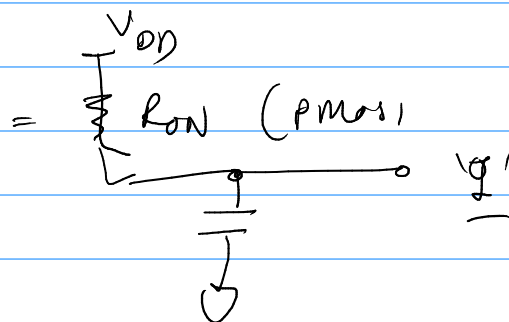
## STATIC CMOS Implementation of Logic expressions.




$$\# \quad Y = \underline{(A + BC)'}$$

$$Min. = \underline{\underline{2 \cdot N}}$$



$$= (A' + B'C')$$

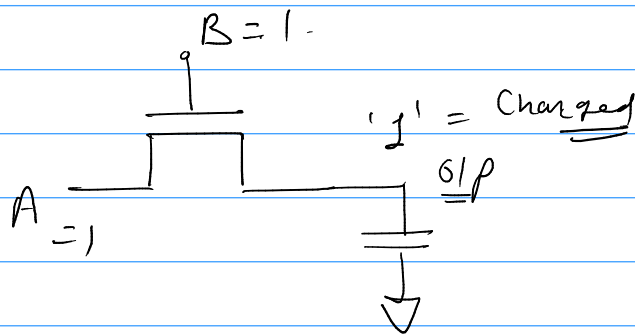

A	B	O/P.
0	0	0
0	1	0
1	0	0
1	1	1

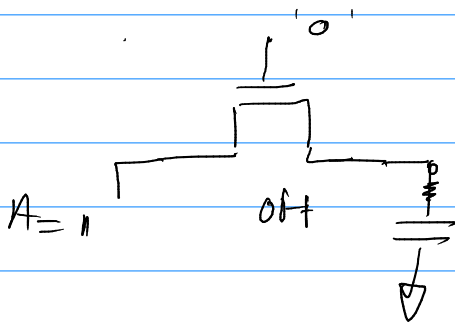

$B = 0$

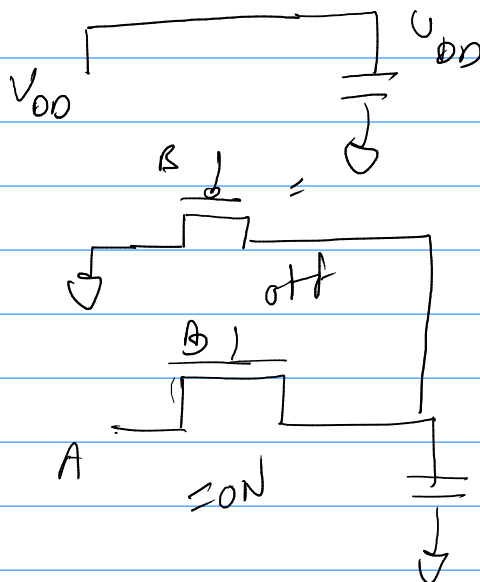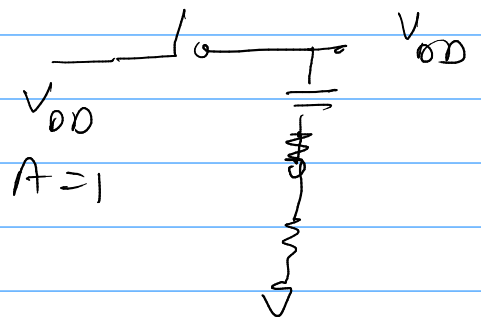

AND

2 x 2



$$\underline{A + B}$$

$$\boxed{A + A'B}$$

$$A'B$$

When  $A = 0$

$$\boxed{O/P = B}$$

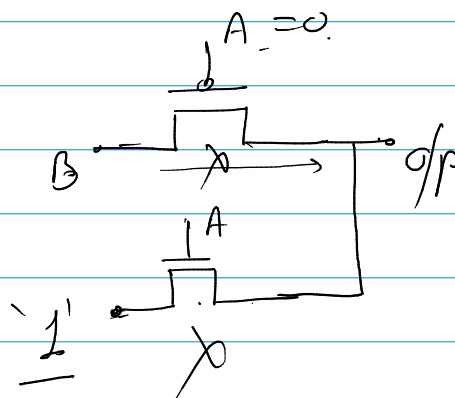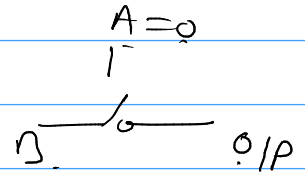


$$\boxed{A'B} + A = \underline{\underline{0}}$$

$$\underline{\underline{A = 1}}$$

$$\underline{\underline{A + B}} \Rightarrow \boxed{A'B} + A = Y$$
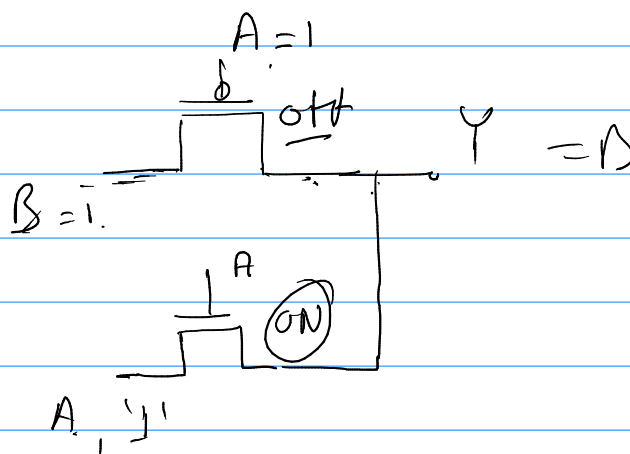
$$\begin{aligned} 1 + 0 &= 1 \\ 1 + 1 &= 1 \end{aligned}$$



$$\boxed{A'B} = 2$$

$$\underline{\underline{A'B + B'A}} = \underline{\underline{xor}}$$