

Computer Organization & Architecture CS 204

Anil Kumar Sao, EECS, IIT Bhilai
anil@iitbhillai.ac.in

Number representation

Number Systems:

- Positive numbers:
- Negative Numbers
 - Sign and Magnitude Representation
 - 1's Complement Representation
 - 2's Complement Representation

Goal of number systems : arithmetic operations

Negative number systems

- Signed system: Simple. Just flip the sign bit
 - 0 = positive
 - 1 = negative

Definitions: Given a positive integer x , we represent $-x$

- 1's complement:
 - Formula: $2^n - 1 - x$
 - i.e. $n=4$, $2^4 - 1 - x = 15 - x$
 - In binary: $(1\ 1\ 1\ 1) - (b_3\ b_2\ b_1\ b_0)$
 - Just flip all the bits.
- 2's complement:
 - Formula: $2^n - x$
 - i.e. $n=4$, $2^4 - x = 16 - x$
 - Just flip all the bits and add 1.

Definitions: 4-Bit Example

id	b_3	b_2	b_1	b_0	Signed	One's	Two's
0	0	0	0	0	0	0	0
1	0	0	0	1	1	1	1
2	0	0	1	0	2	2	2
3	0	0	1	1	3	3	3
4	0	1	0	0	4	4	4
5	0	1	0	1	5	5	5
6	0	1	1	0	6	6	6
7	0	1	1	1	7	7	7
8	1	0	0	0	-0	-7	-8
9	1	0	0	1	-1	-6	-7
10	1	0	1	0	-2	-5	-6
11	1	0	1	1	-3	-4	-5
12	1	1	0	0	-4	-3	-4
13	1	1	0	1	-5	-2	-3
14	1	1	1	0	-6	-1	-2
15	1	1	1	1	-7	-0	-1

Given n-bits, what is the range of numbers in each system?

- 3 bits:
 - Signed: -3 , 3
 - 1's: -3 , 3
 - 2's: -4 , 3
- 5 bits:
 - Signed: -15, 15
 - 1's: -15, 15
 - 2's: -16, 15
- 6 bits
 - Signed: -31, 31
 - 1's: -31, 31
 - 2's: -32, 31
- Given 8 bits
 - Signed: -127, 127
 - 1's: -127, 127
 - 2's: -128, 127

**Formula for
calculating the
range →**

Signed & 1's: $-(2^{n-1} - 1) , (2^{n-1} - 1)$
2's: $-2^{n-1} , (2^{n-1} - 1)$

Arithmetic Operations: 2's Complement

Input: two positive integers x & y ,

1. We represent the operands in two's complement.
2. We sum up the two operands and ignore bit n .
3. The result is the solution in two's complement.

Arithmetic

2's complement

$$x + y$$

$$x + y$$

$$x - y$$

$$x + (2^n - y) = 2^n + (x - y)$$

$$-x + y$$

$$(2^n - x) + y = 2^n + (-x + y)$$

Arithmetic Operations: Example: $4 - 3 = 1$

$$4_{10} = 0100_2$$

$$3_{10} = 0011_2$$

$$-3_{10} \rightarrow 1101_2$$

$$\begin{array}{r} 0100 \\ + 1101 \\ \hline \end{array}$$

10001 $\rightarrow 1$ (after discarding extra bit)

We discard the extra 1 at the left which is 2^n from 2's complement of -3. Note that bit b_{n-1} is 0. Thus, the result is positive.

Arithmetic Operations: Example: $-4 + 3 = -1$

$4_{10} = 0100_2$ $-4_{10} \rightarrow$ Using two's comp. $\rightarrow 1011 + 1 = 1100_2$
 $3_{10} = 0011_2$ (Invert bits)

$$\begin{array}{r} 1100 \\ + 0011 \\ \hline \end{array}$$

$1111 \rightarrow$ Using two's comp. $\rightarrow 0000 + 1 = 1$,
so our answer is -1

If left-most bit is 1, it means that we have a negative number.

Arithmetic Operations: Example: $4 - 3 = 1$

$$4_{10} = 0100_2$$

$$3_{10} = 0011_2$$

complement


$$-3_{10} \rightarrow 1100_2 \text{ in one's}$$

$$\begin{array}{r} 0100 \\ + 1100 \\ \hline 1,0000 \end{array}$$


0001(after deleting 2^n-1)

If an end carry occurs, add 1 to least significant digit.


4-bit adder/subtractor

 

Carry look ahead adder


 


Carry look ahead adder

 


Decoder

  - Circuit that takes an n -bit number as input and uses it to select exactly one of the 2^n output lines





Multiplexers

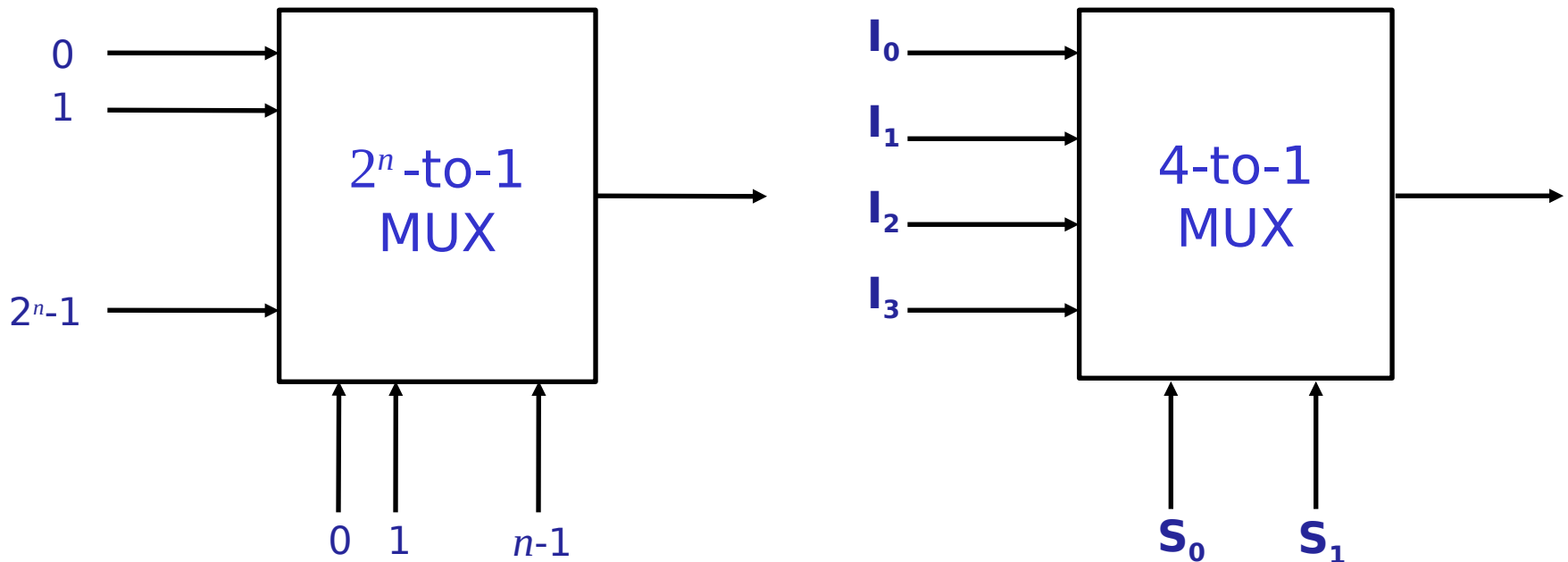- Multiplexer is a circuit with 2^n data inputs and one data output and n control lines to select one of the data inputs
- The selected input is gated (i.e. routed) to the output





Demultiplexers

  
- Inverse of a multiplexer
- Routes its single input signal to one of 2^n outputs, depending on the values of n control lines




1-bit ALU

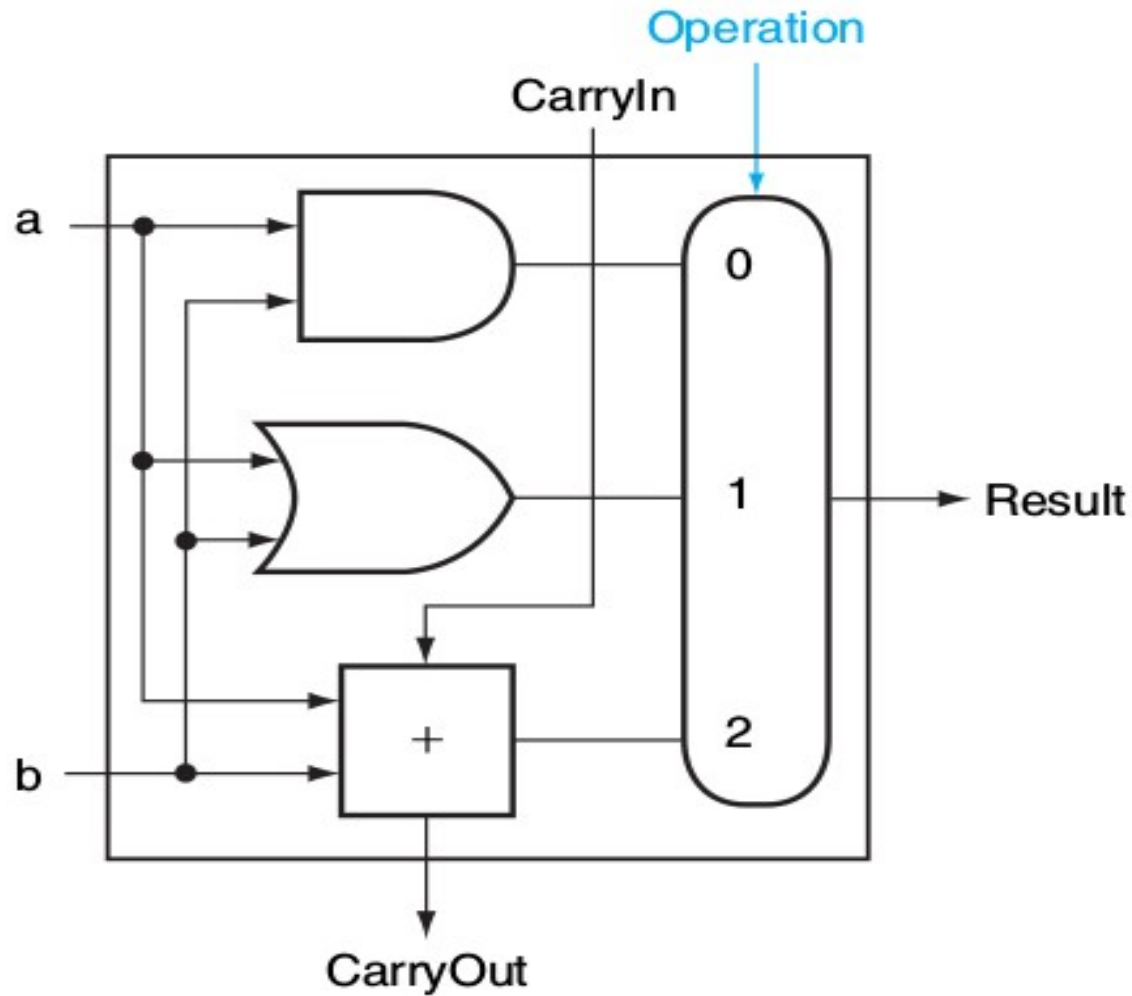

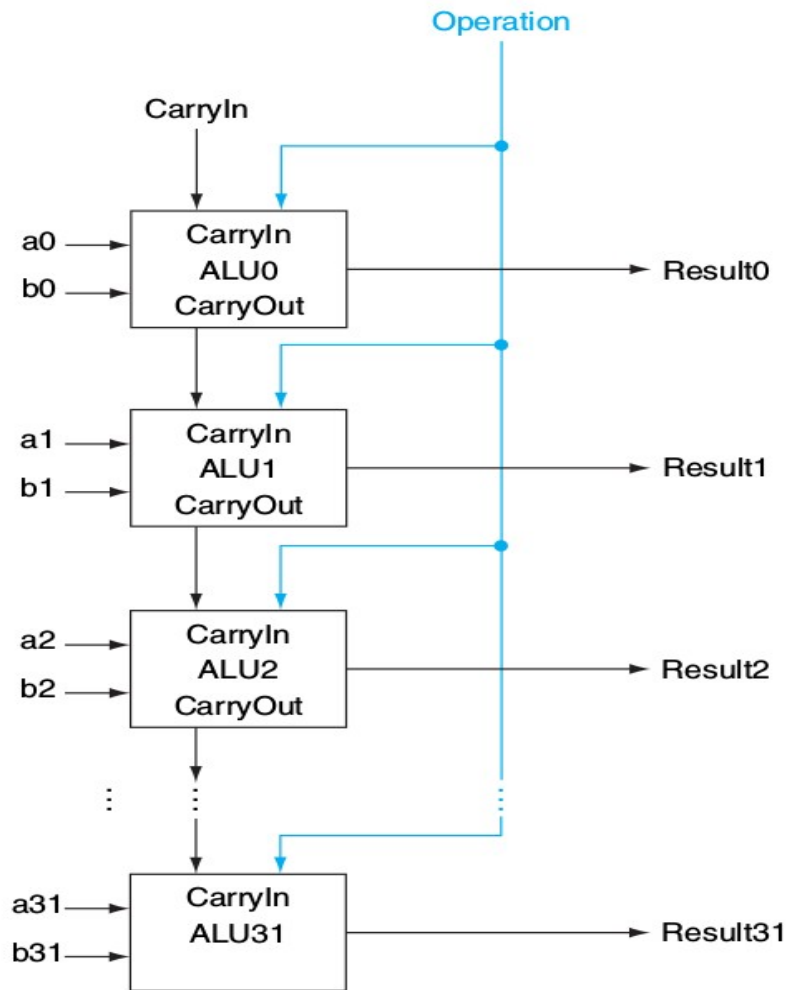

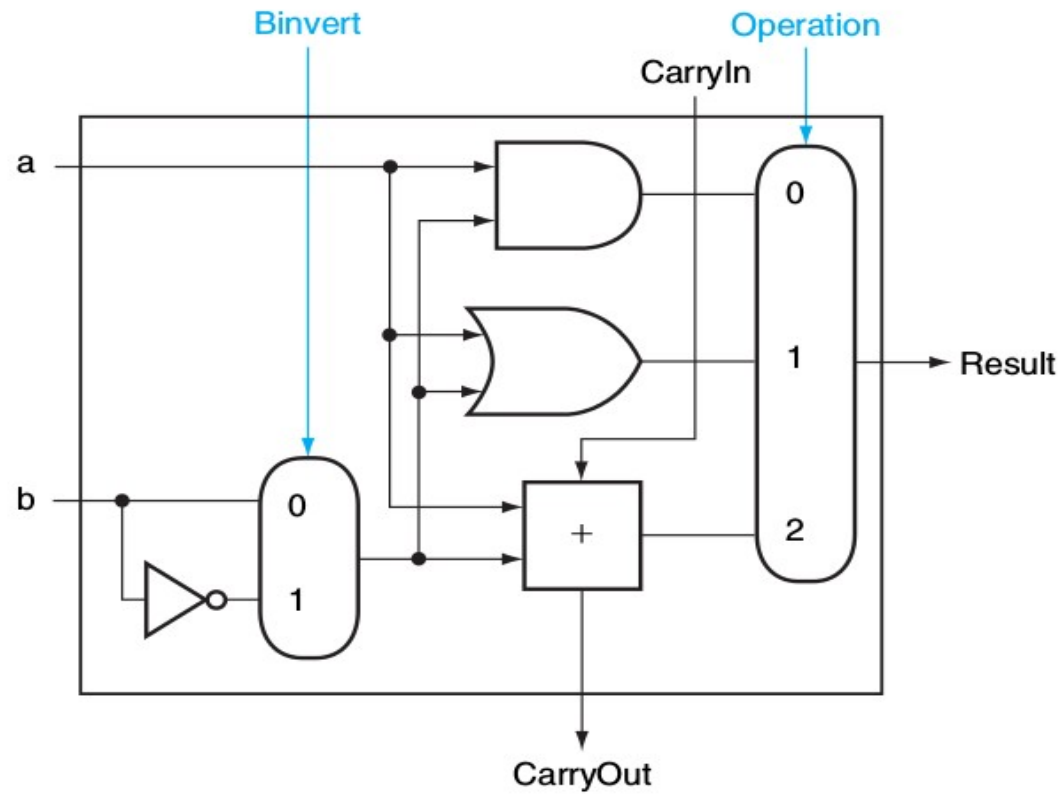

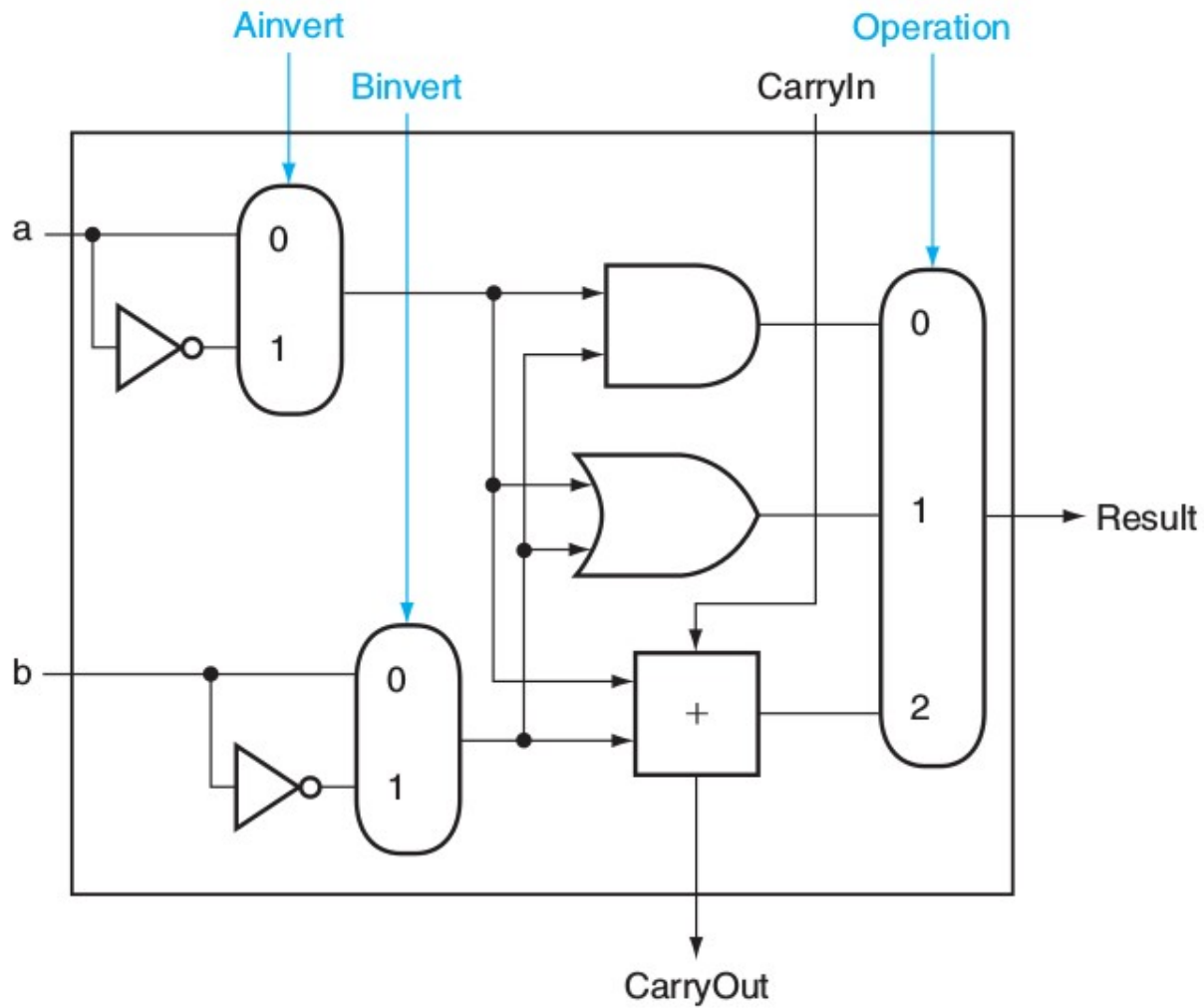

Digital Ckt for Multiplication

Multiplication of Unsigned Integers

- Two operands: **Multiplier** and **Multiplicand**

Multiplicand → 2 1 3 x 1 2 5 ← Multiplier

1065 ← Partial product for digit 0

426 ← Partial product for digit 1

213 ← Partial product for digit 2

26625 ← Product

- Each **partial products** are placed in such a way that each are **shifted** according to their weight in the multiplier
- Long-hand-multiplication** (paper-and-pencil method)

n-bit Binary Multiplication

- The product of two *n*-bit integers leads to *2n*-bit product

$$\begin{array}{r} 13 \times 11 \\ 1101 \times 1011 \\ \hline 1101 \leftarrow PP_0 \\ 1101 \leftarrow PP_1 \\ 0000 \leftarrow PP_2 \\ 1101 \leftarrow PP_3 \\ 111000 \\ \hline 10001111 \leftarrow P \\ \hline \end{array}$$


4-bit Multiplication

- X_{3-0} : $x_3 x_2 x_1 x_0$ Multiplicand
- Y_{3-0} : $y_3 y_2 y_1 y_0$ Multiplier

								$x_3 x_2 x_1 x_0$	\times	$y_3 y_2 y_1 y_0$		
								$x_3 y_0$	$x_2 y_0$	$x_1 y_0$	$x_0 y_0$	← PP_0
								$x_3 y_1$	$x_2 y_1$	$x_1 y_1$	$x_0 y_1$	← PP_1
								$x_3 y_2$	$x_2 y_2$	$x_1 y_2$	$x_0 y_2$	← PP_2
								$x_3 y_3$	$x_2 y_3$	$x_1 y_3$	$x_0 y_3$	← PP_3
p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	← P				



- Multiplier is designed using **AND gates** and **1-bit Full Adder circuits**
- **Combinational array multiplier circuit**

Combinational Array Multiplier Circuit

 


- Uses ripple carry adder

Full Adder

 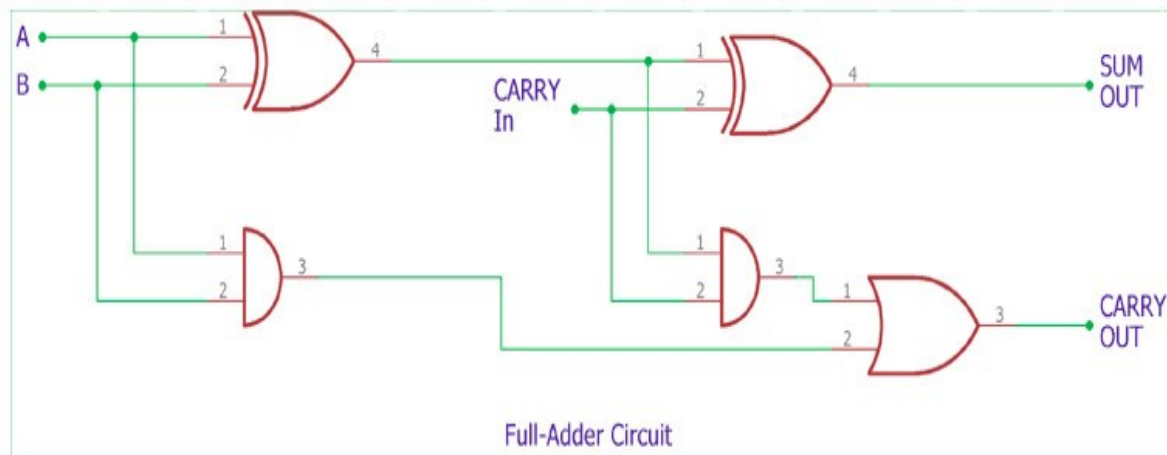

Combinational Array Multiplier

 - Propagation delay through
 - AND gate : $1 t_{pd}$ 1-bit Full Adder: $2 t_{pd}$



- Latency of 4-bit multiplication: $17 t_{pd}$

Latency of n -bit Multiplication

- Multiplication of two n -bit multiplication involve
 - $(n-1)$ levels of addition
 - n Full adders at each level
- Input for first level of addition is obtained at: $1 t_{pd}$
- First input for 2nd level of addition is obtained at: $5 t_{pd}$
- First input for 3rd level of addition is obtained at: $9 t_{pd}$
- Total latency: $4n-7 + 2n = (6n-7) t_{pd}$

Signed Integer Multiplication

- Consider: -ve multiplier and +ve multiplicand

$$\begin{array}{r}
 5 \times -3 \\
 0101 \times 1101 \\
 \hline
 00000101 \longleftarrow PP_0 \\
 00000000 \longleftarrow PP_1 \\
 000101 \longleftarrow PP_2 \\
 00101 \longleftarrow PP_3 \\
 0111100 \\
 \hline
 01010001 \longleftarrow P \text{ (-15)?} \\
 \hline
 \end{array}$$


- Does not lead to correct solution
- For negative multiplier case, form 2's complement of both multiplier and multiplicand and proceed as in the case of positive multiplier

Signed Integer Multiplication

- Consider: -ve multiplier and +ve multiplicand

$$\begin{array}{r}
 5 \times -3 \\
 0101 \times 1101 \\
 \hline
 1011 \times 0011 \quad \text{2's complement: } (-5 \times 3) \\
 \hline
 11111011 \leftarrow PP_0 \\
 1111011 \leftarrow PP_1 \\
 000000 \leftarrow PP_2 \\
 00000 \leftarrow PP_3 \\
 \textcolor{blue}{1111110} \\
 \hline
 1 \quad 11110001 \leftarrow P \text{ (-15)} \\
 \hline
 \end{array}$$


Combinational Array Multiplier Circuit

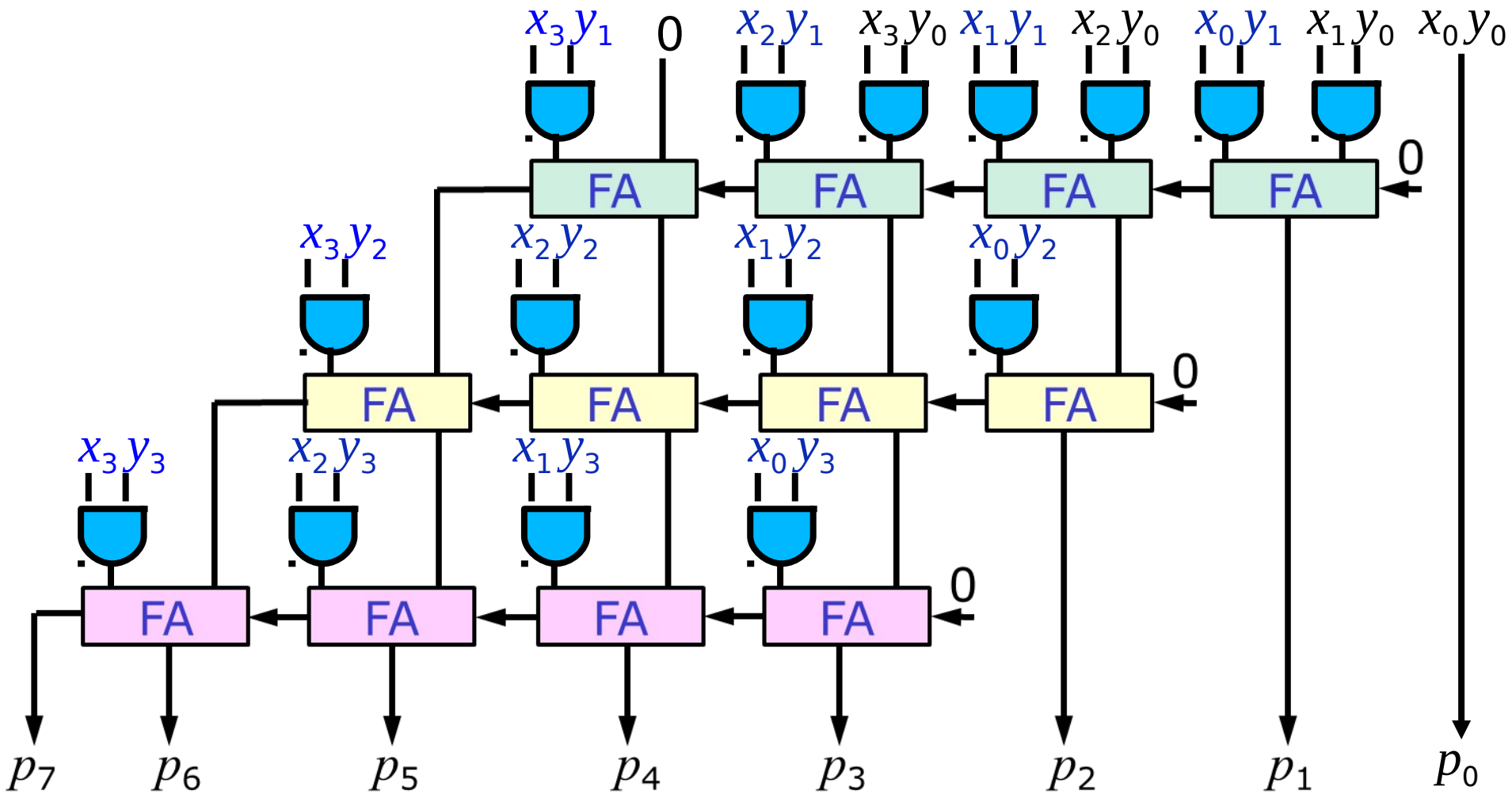


- Uses ripple carry adder

Sequential algorithm for n -bit Multiplication
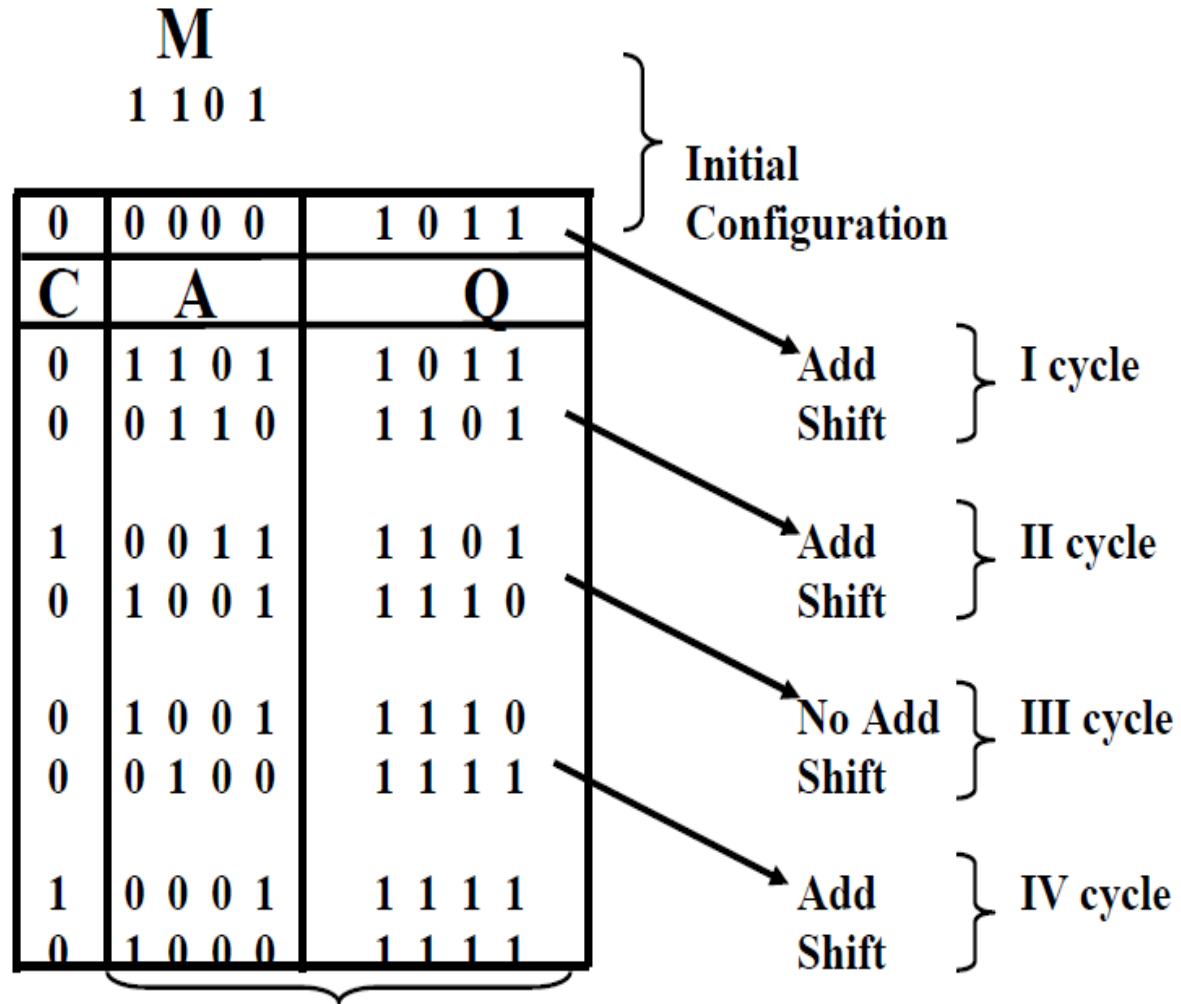
$$\begin{array}{r}
 13 \times 11 \\
 1101 \times 1011 \\
 \hline
 1101 \quad \leftarrow PP_0 \\
 1101 \quad \leftarrow PP_1 \\
 0000 \quad \leftarrow PP_2 \\
 1101 \quad \leftarrow PP_3 \\
 111000 \\
 \hline
 10001111 \quad \leftarrow P
 \end{array}$$



Sequential ckt for n -bit Multiplication

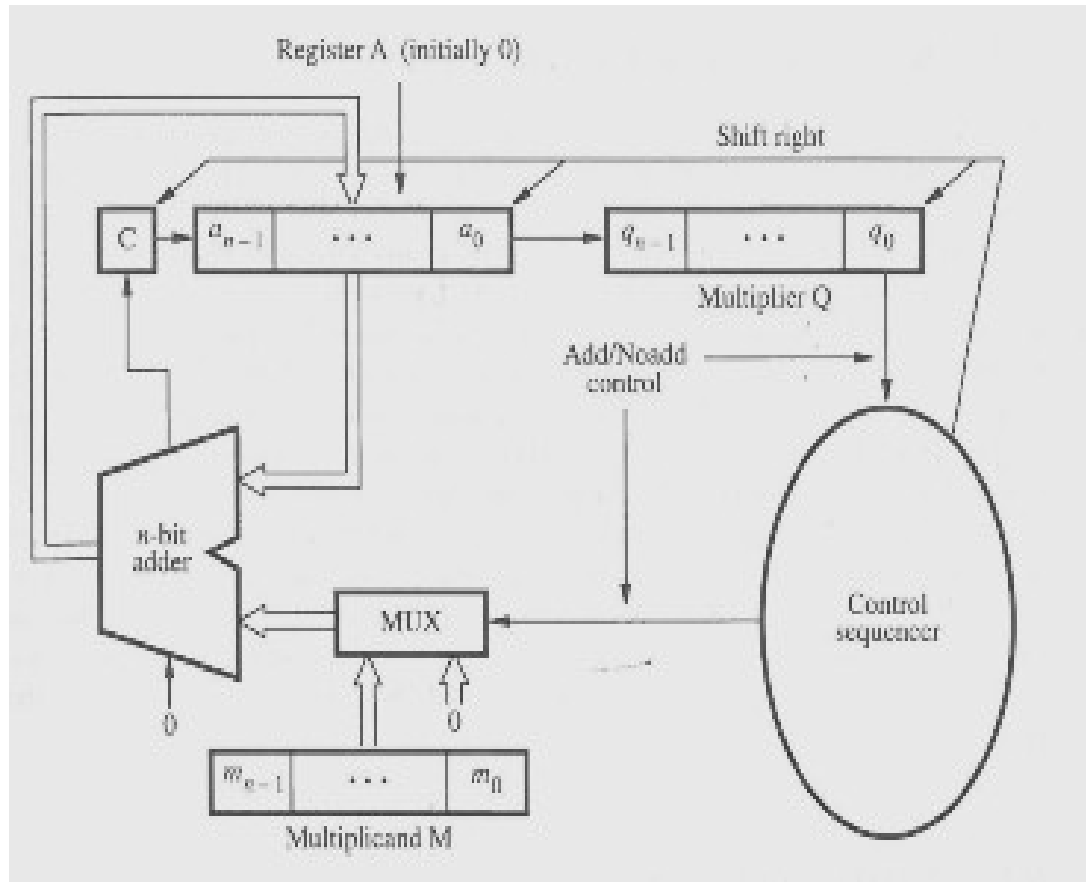

M			
1 1 0 1			
0	0 0 0 0	1 0 1 1	Initial Configuration
C	A	Q	
0	1 1 0 1	1 0 1 1	Add Shift } I cycle
0	0 1 1 0	1 1 0 1	
1	0 0 1 1	1 1 0 1	Add Shift } II cycle
0	1 0 0 1	1 1 1 0	
0	1 0 0 1	1 1 1 0	No Add Shift } III cycle
0	0 1 0 0	1 1 1 1	
1	0 0 0 1	1 1 1 1	Add Shift } IV cycle
0	1 0 0 0	1 1 1 1	

Booth Recording of Multiplier Operand

- This approach treat both positive and negative integers (or operands) in 2's compliment form uniformly
- It records (encodes) the multiplier operand in Booth multiplier form
- Booth multiplier recording table:

Multiplier		Version of multiplicand selected by bit i
bit i	bit $i-1$	
0	0	0x multiplicand
0	1	+1 x multiplicand
1	0	-1 x multiplicand
1	1	0x multiplicand

2's
compliment 1 0 1 1 1 0

Booth recording **-1**

Booth Recording of Multiplier Operand

- This approach treat **both positive and negative integers** (or operands) in 2's compliment form **uniformly**
- It records (encodes) the multiplier operand in Booth multiplier form
- **Booth multiplier recording table:**

Multiplier		Version of multiplicand selected by bit i
bit i	bit $i-1$	
0	0	0x multiplicand
0	1	+1 x multiplicand
1	0	-1 x multiplicand
1	1	0x multiplicand

2's
complimen
t

1 0 1 1 1 0
 $i \quad i-1$

Booth
recording

0 -1

Booth Recording of Multiplier Operand

Multiplier		Version of multiplicand selected by bit i
bit i	bit $i-1$	
0	0	0x multiplicand
0	1	+1 x multiplicand
1	0	-1 x multiplicand
1	1	0x multiplicand

2's
compliment $1\ 0\ 1\ 1\ 1\ 0$

Booth
recording $0\ 0\ -1$

Booth Recording of Multiplier Operand

Multiplier		Version of multiplicand selected by bit i
bit i	bit $i-1$	
0	0	0x multiplicand
0	1	+1 x multiplicand
1	0	-1 x multiplicand
1	1	0x multiplicand

2's
complimen
t

Booth
recording

i $i-1$
 1 0 1 1 1 0
 1 0 0 -1

Booth Recording of Multiplier Operand

Multiplier		Version of multiplicand selected by bit i
bit i	bit $i-1$	
0	0	0x multiplicand
0	1	+1 x multiplicand
1	0	-1 x multiplicand
1	1	0x multiplicand

2's
complimen
t

i $i-1$
1 0 1 1 1 0


Booth
recording

-1 1 0 0 -1


Signed Integer Multiplication

- Consider: -ve multiplier and +ve multiplicand
- Booth recording of multiplier
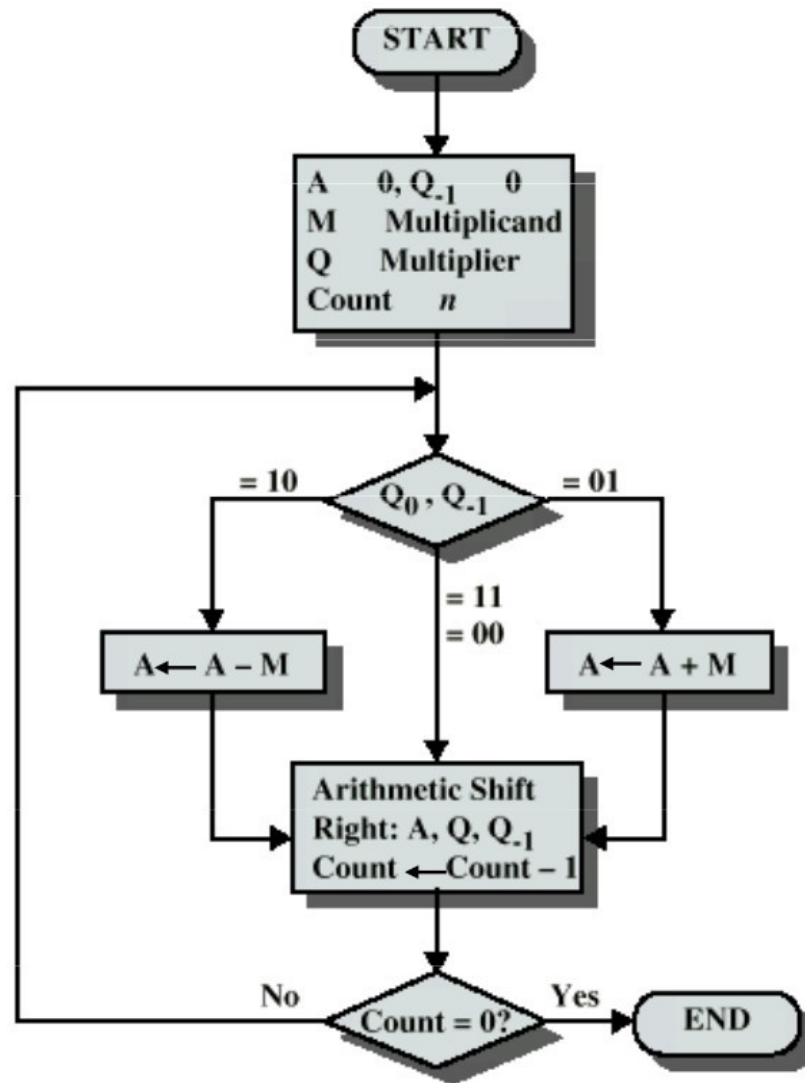
$$\begin{array}{r}
 \begin{array}{r}
 5 \times -3 \\
 0101 \times 1101 \\
 \hline
 0101 \times 0-1+1-1 \\
 \hline
 11111011 \leftarrow \text{2's compliment of } 0101 \\
 0000101 \\
 111011 \leftarrow \text{2's compliment of } 0101 \\
 00000 \\
 1110110 \\
 0 \\
 \hline
 111110001
 \end{array}
 \end{array}$$



Multiplier Bit-Pair Recoding

 

(a) Example of bit-pair recoding derived from Booth recoding

Multiplier bit-pair		Multiplier bit on the right $i-1$	Multiplicand selected at position i
$i+1$	i		
0	0	0	$0 \times M$
0	0	1	$+1 \times M$
0	1	0	$+1 \times M$
0	1	1	$+2 \times M$
1	0	0	$-2 \times M$
1	0	1	$-1 \times M$
1	1	0	$-1 \times M$
1	1	1	$0 \times M$

Multiplication with Carry Save Addition of Summands

Carry Save Addition (CSA) of Summands

- In combinational array (CA) multiplication logic, the n partial products i.e. n summands are added sequentially
- Can we do the parallel addition of summands?
- **Idea:**
 - Avoid the carries ripple along rows
 - Carries can be saved and introduced into the next row
- Example:


$$\begin{array}{r} 11011 \\ 01010 \\ \hline \text{S } 10001 \\ \text{C } 010100 \\ \hline \end{array}$$

CSA of Summands

- Group the summands in **threes** and then perform CSA
- This generates the further set of **sum (S)** and **carry (C)** vectors
- Continue this process until there are only **two vectors (summands)** remaining
- **The final summands are added in a RCA or CLA** to produce desired product
- Note:
 - Each partial products are shifted versions of multiplicands
 - Partial products, S and C vectors are considered as summands
 - Each of these summands are shifted versions
- Multiplication using CSA can be applied to both unsigned and signed integer

Illustration of CSA

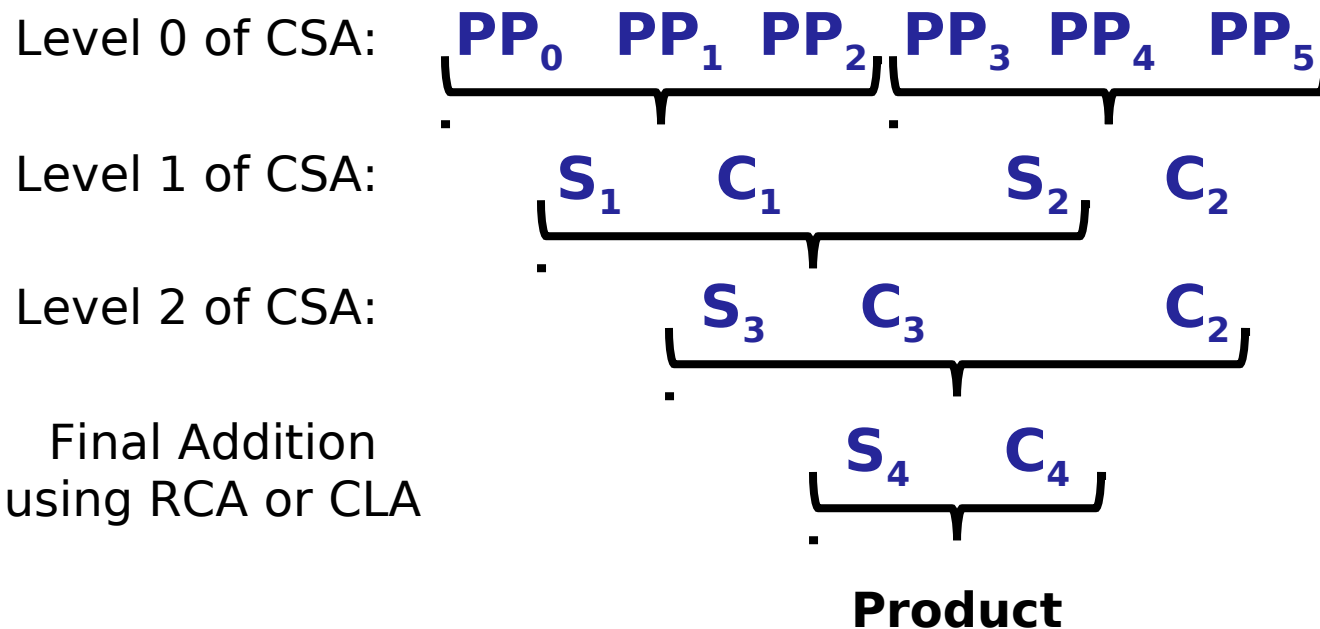
- Consider 6-bit multiplication that results in 6 partial products (summands)



4-bit Unsigned Multiplication using CSA

$$\begin{array}{r} 13 \times 11 \\ 1101 \times 1011 \\ \hline 00001101 \leftarrow PP_0 \\ 00011010 \leftarrow PP_1 \\ 00000000 \leftarrow PP_2 \\ 01101000 \leftarrow PP_3 \end{array}$$

4-bit Unsigned Multiplication using CSA

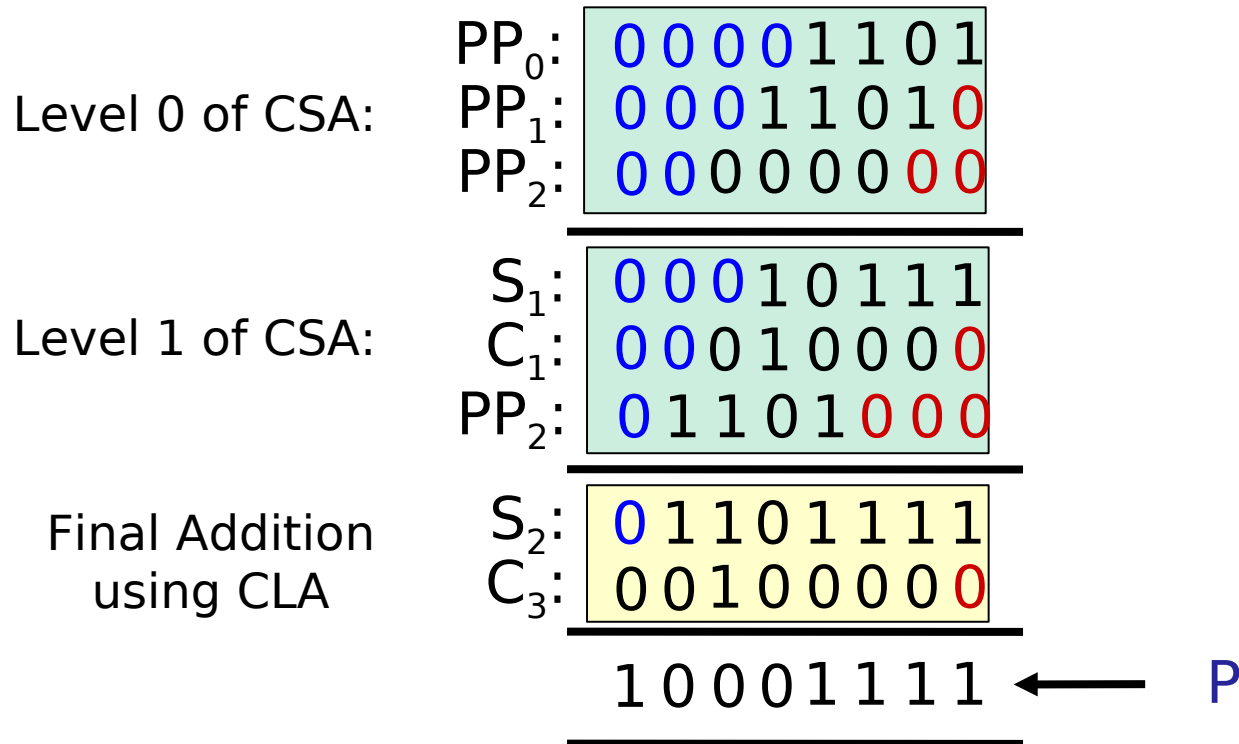


4-bit Unsigned Multiplication using CSA


• X_{3-0} : $x_3 x_2 x_1 x_0$ **Multiplicand**

• Y_{3-0} : $y_3 y_2 y_1 y_0$ **Multiplier**


Level 0 of CSA:

 

4-bit Unsigned Multiplication using CSA

 

4-bit Unsigned Multiplication using CSA

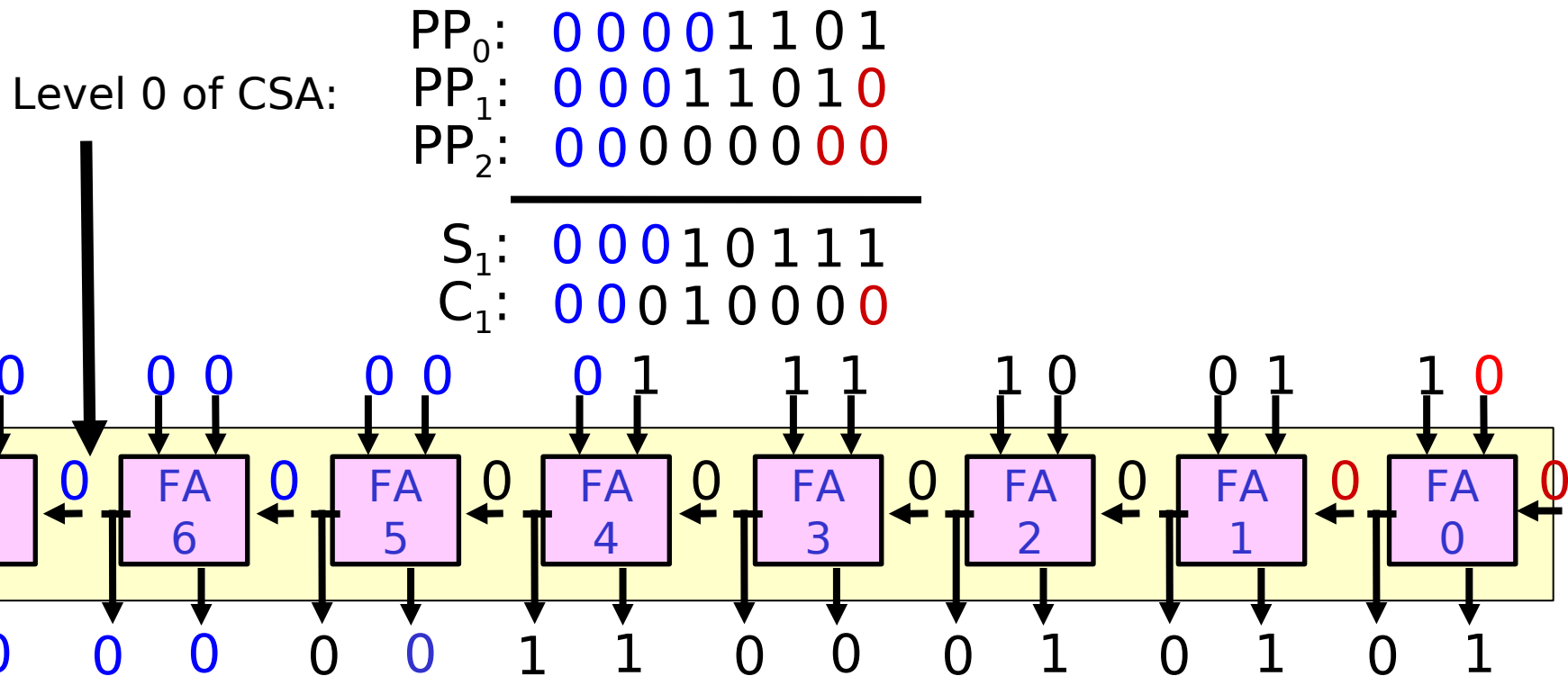

- Propagation delay for CSA (given the summands): $2 t_{pd}$
- S and C vectors are generated in 1 full adder delay

Latency of n -bit Multiplication using CSA

- We have seen that the latency of combinational array multiplication is of two n -bit multiplication: $(6n-7) t_{pd}$
- Partial products are generated at : $1 t_{pd}$
- Delay through full adder (FA) : $2 t_{pd}$
- Hence, delay for CSA at a level i is : $2 t_{pd}$
- Let m be the number of CSA levels
- Delay through m CSA levels : $2m t_{pd}$
- Last level uses $2m$ -bit adder with l -bit CLA
- So, addition in the last stage has delay : $\left(2\left(\frac{2n}{l}\right) + 2\right) t_{pd}$
- Total latency: $1 + 2m + \left(\frac{4n}{l}\right) + 2 = \left(2m + \left(\frac{4n}{l}\right) + 3\right) t_{pd}$
- When $n=4$, $m=2$ and let $l=4$ for CLA
 - Latency = $11 t_{pd}$

Latency of n -bit Multiplication using CSA

- We have seen that the latency of combinational array multiplication is of two n -bit multiplication: $(6n-7) t_{pd}$
- Partial products are generated at : $1 t_{pd}$
- Delay through full adder (FA) : $2 t_{pd}$
- Hence, delay for CSA at a level i is : $2 t_{pd}$
- Let m be the number of CSA levels
- Delay through m CSA levels : $2m t_{pd}$
- Last level uses $2m$ -bit adder with l -bit CLA
- So, addition in the last stage has delay : $\left(2\left(\frac{2n}{l}\right) + 2\right) t_{pd}$
- Total latency: $1 + 2m + \left(\frac{4n}{l}\right) + 2 = \left(2m + \left(\frac{4n}{l}\right) + 3\right) t_{pd}$
- When $n=4$, $m=2$ and let $l=4$ for CLA
 - Latency = $11 t_{pd}$

Latency of n -bit Multiplication using CSA

- We have seen that the latency of combinational array multiplication is of two n -bit multiplication: $(6n-7) t_{pd}$
- Partial products are generated at : $1 t_{pd}$
- Delay through full adder (FA) : $2 t_{pd}$
- Hence, delay for CSA at a level i is : $2 t_{pd}$
- Let m be the number of CSA levels
- Delay through m CSA levels : $2m t_{pd}$
- Last level uses $2m$ -bit adder with l -bit CLA
- So, addition in the last stage has delay : $\left(2\left(\frac{2n}{l}\right) + 2\right) t_{pd}$
- Total latency: $1 + 2m + \left(\frac{4n}{l}\right) + 2 = \left(2m + \left(\frac{4n}{l}\right) + 3\right) t_{pd}$
- When $n=4$, $m=2$ and let $l=4$ for CLA
 - Latency = $11 t_{pd}$

Issue in CSA

- How to determine the m , the number of levels in CSA
- In general: $m \approx 1.7 \log_2 k - 1.7$ where k is number of initial summands